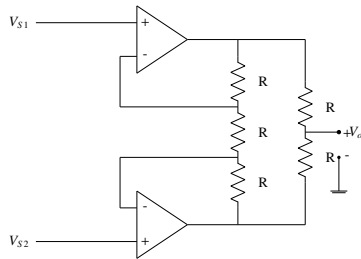


Gate 2023- Instrumentation Engineering

EE23BTECH11037 - M Esha*

Question 59: The op amps in the circuit are ideal. The input signals are $V_{S1} = 3 + 0.10 \sin(300t)$, V and $V_{S2} = -2 + 0.11 \sin(300t)$ V. The average value of the voltage V_0 is _____ volts (rounded off to two decimal places).



(GATE IN 2023)